



PAMANTASAN NG LUNGSOD NG MAYNILA
(University of the City of Manila)
Intramuros, Manila

Microprocessor Lab

Laboratory Activity No. 1
Familiarization with TinkerCAD



Score

Submitted by:
Dela Cruz, Alfonso Rafael C.
Saturday 1pm to 4pm / Block 2

Date Submitted
16-09-2023


Submitted to:
Engr. Maria Rizette H. Sayo

1. Exercise


- A process in Tinkercad where we can develop electronic circuits that can be quickly updated, modified, and tested is called Breadboarding.
- In Tinkercad, Simulation tests the working of the circuits and the components.
- The device used to assemble and connect the various components is known as Breadboard.
- In an electronic circuit with LED, the positive end of the circuit should be connected to Anode and negative end should be connected to Cathode of the LED.
- A Resistor is used to restrict the flow of current to electrical components.

2. Label the following:

- Anode and Cathode in a LED

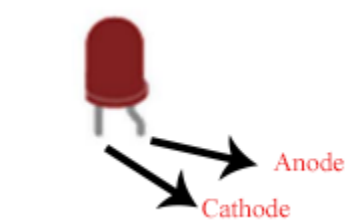

- Different parts of breadboard

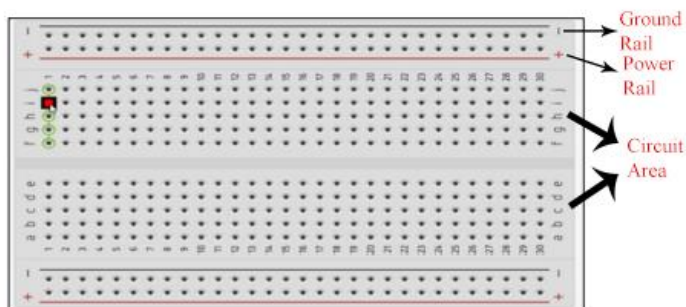

- List the electronic components used in a circuit assembly.

Analog I/O

- Arduino Uno R3
- Breadboard
- LED
- Resistor
- Wires
- Potentiometer

Digital I/O

- Arduino Uno R3
- Breadboard
- LED
- Resistor
- Wires